

ASSIGNMENT 5

Due date: Oct 28, 2025 (4 PM)

Unless otherwise specified all op amps are ideal.

Relevant Class Notes Transfer Functions §7, 9.1 Operational Amplifiers (§ 2.4, 3, 4, 5.1, 8.1)	Assessment Criteria Apply one or more procedure(s) to a problem. Analyze a problem and obtain a correct result. Write a MATLAB script to analyze a problem. Interpret observations / results.
References to Prior Assignments Q3 builds upon Assignment 3 Q4 & Assignment 4 Q3.	

Manage your time. Having problems with the assignment? Discuss them with the instructor!

Attachment05.zip accompanies this assignment and contains needed MATLAB files.

1. (2.5/10)

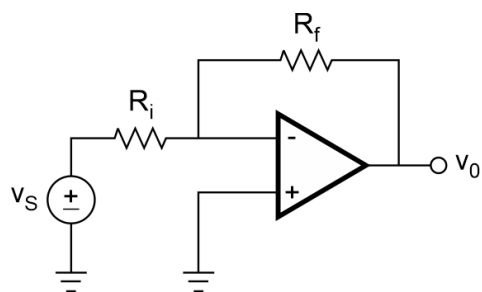


Figure 1

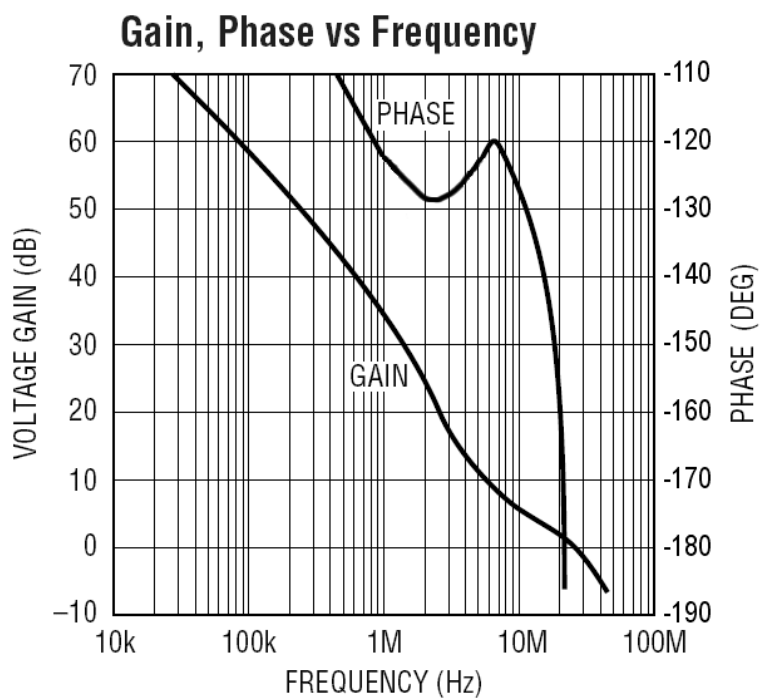


Figure 2

You need to build the amplifier (operational circuit) shown in Figure 1 and are considering using an op amp having the open-loop frequency response shown in Figure 2.

You may assume that at frequencies below 30kHz that:

- The system loop gain is very large ($\gg 1$)
- The op-amp phase response monotonically $\rightarrow 0^\circ$ as frequency $\rightarrow 0$

What are the restrictions on the amplifier gain¹ for the system to be stable with a minimum phase margin of 45°?

Recall:

- Amplifier gain is a low-frequency characteristic. Given the above information, you do not need to see the open-loop frequency response down to low frequency.
- Questions of stability are high-frequency phenomenon. Hence the frequency range shown in Figure 2.
- Stability analysis involves analyzing the system loop gain. In actuality, the op-amp frequency response is the loop-gain frequency response when $\beta = 1$.)

2. (2/10)

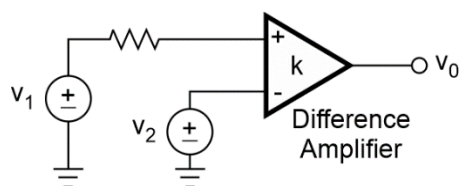


Figure 3

Q2.p, which accompanies this assignment, simulates a realistic difference amplifier with finite common mode rejection, as shown in Figure 3. Determine the amplifier's common-mode rejection (CMR) by performing two experiments, where you excite the amplifier with a differential signal then with a common-mode signal. Attach your MATLAB code.

3. (4.5/10)

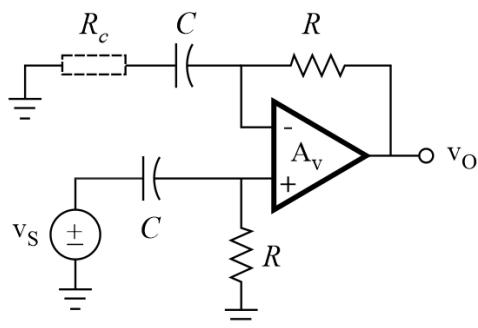


Figure 4. Differentiator (Noninverting)

A *differentiator*, shown in Figure 4, followed by a *comparator* is useful for detecting an event for which the slope exceeds a given value – for example, detection of the R-wave in an electrocardiogram, as shown in Figure 5.

Unfortunately, the differentiator circuit exhibits stability problems but can be stabilized by inserting a compensating resistance (R_c).

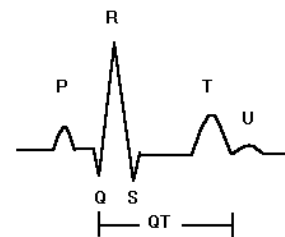


Figure 5. ECG Signal

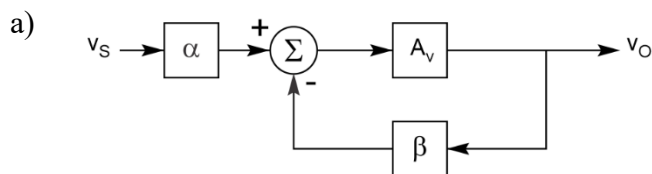


Figure 6

The circuit may be represented with the block diagram shown in Figure 6, which is the classical negative-feedback diagram, augmented with the α block, which accounts for V_S not going directly to the op-amp '+' terminal. The resulting closed-loop response is:

$$A_{CL}(s) = \frac{V_O(s)}{V_S(s)} = \frac{\alpha(s)A_v(s)}{1 + A_v(s)\beta(s)}$$

¹ Do not confuse the amplifier gain with the op-amp gain. The amplifier gain is the operational circuit's closed-loop static gain, when the system loop gain is $\gg 1$, and is expressed as a single real number.


Use the feedback-analysis approach to:

- i) Determine α and β in Figure 6 for the system in Figure 4 when R_c in series with C is represented as an equivalent impedance, Z . (Leave your answer in terms of Z .)
- ii) Setting $R_c = 0$, use the results from (i) to determine the ideal operational equation (i.e., assuming an ideal op amp) as a function of R and C .

b) With $R_c = 0$ and $A_v(s) = \frac{A_0}{s\tau_0 + 1}$, the system transfer function is

$$A_{CL}(s) = \frac{sRCA_0}{(sRC + 1)(s\tau_0 + 1) + A_0}$$

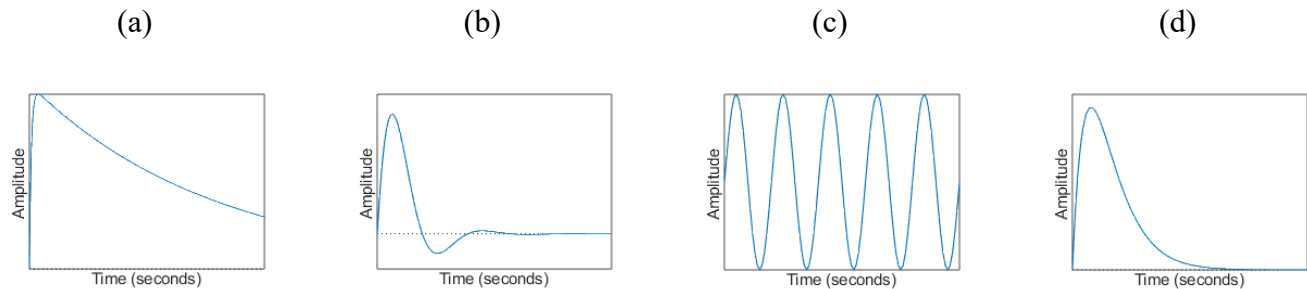- i) Show that the transfer function damping ratio $\rightarrow 0$ as $A_0 \rightarrow \infty$. (Refer to class notes on *Transfer Functions* and the section on 2nd-order systems.)
- ii) In terms of the natural modes of response of a system, which of the following cases corresponds with the scenario in (i)? (Select all that apply.)



c) *Q3c.p*, which accompanies this assignment, evaluates the system transfer function for a set of component values. Let $C = 560\text{nF}$, $R = 243\text{k}\Omega$, $A_0 = 1 \times 10^5 \text{V/V}$, and $\tau_0 = 1/(20\pi)$ seconds. Using MATLAB, find a compensating resistance, R_c , that yields the fastest step response without making the system be underdamped.

- Use *pzmap* to assess your choice of R_c .
- Plot the system step response over 3ms for the uncompensated and compensated cases.
- Limit your component selection to standard resistor values from the 1% line. (See the Appendix in the class notes on *Electronic Circuits* for standard passive component values.) I recommend that you find the correct value by probing values using a manual and systematic approach. Tip: R_c controls the system damping ratio.

d) Use *Q3d_primer.m* to help you get started. Plot superimposed frequency responses of:

- The ideal system transfer function ($A_{CL \text{ ideal}}$)
- The op-amp gain (A_v)
- The loop gain ($A_v\beta$)
- The transfer function of the compensated system (A_{CL})

Briefly comment on how $|A_{CL}(j\omega)|$ compares to $|A_{CL \text{ ideal}}(j\omega)|$ in relation to the loop-gain magnitude response and $|A_v(j\omega)|$. In particular:

- Under what condition is the desired $|A_{CL}(j\omega)|$ achieved?
- What determines the high-frequency performance of $|A_{CL}(j\omega)|$?

e) Over what frequency range does the compensated circuit act as a differentiator? Briefly justify your conclusion.

4. (1/10)

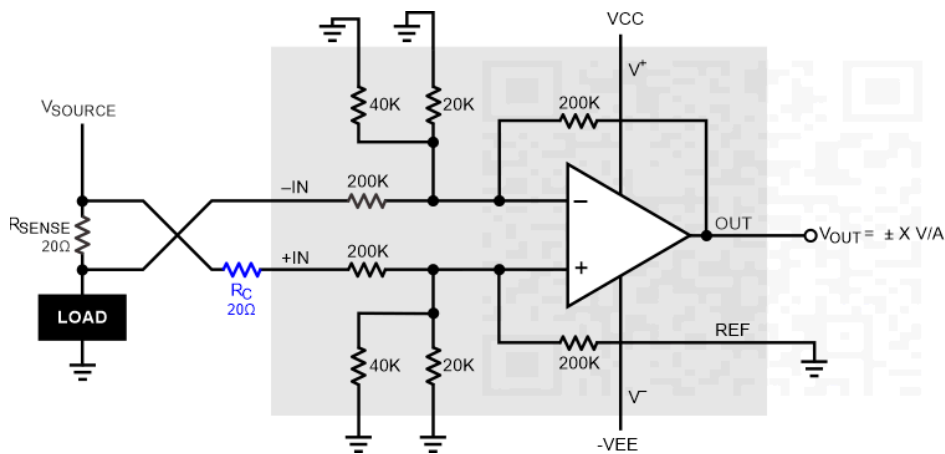


Figure 7. Precision Current Monitor

Op Amp Parameters	
A_v	Not available
GBW	8 MHz
V_{os}	5 mV (max)
I_B	$\pm 2\text{nA}$ (max)
CMR	83 dB (min)
SR	4 V/ μs
V_{SAT}	Rail-to-rail

The I.C. shown in Figure 7 is a voltage difference amplifier incorporating a precision op amp and a matched resistor network. The circuit illustrates an application of the I.C. in a precision current monitor. Op amp parameters are shown in the accompanying table.

Circuit operation: current through the load is determined by monitoring the voltage drop across R_{SENSE} . Assuming zero source resistance the output voltage is proportional to current with sensitivity X volts per ampere of load current.

Question: Assuming zero source resistance, what is the purpose of R_C on the +IN input? (No formal circuit analysis necessary.) Assume that the load resistance $\gg R_{SENSE}$. Select one of the following options.

- To maintain op-amp CMR
- To maintain circuit CMR
- To allow the output to swing at the op-amp SR specification
- To allow the output voltage to swing beyond $\pm V_{SAT}$
- To minimize output offset error due to V_{OS}
- (a) and (b)
- None of the above

5. (0.5/10) Bonus

Report the amount of time spent on this assignment.

Relevant MATLAB function(s):

You will have to use functions introduced in previous assignments.